 


Kourosh Alinaghi

810101476

1)


(g)



b)

worst case. NAND delay =  $3 \times 4 = 12 \text{ ns}$


3input NAND:

 

Worst case delay of the circuit =  $24 \text{ ns}$

c) when  $\{S, R\} = \{0, 0\} \Rightarrow Q \text{ and } \bar{Q} \text{ are } 1 \Rightarrow \text{illegal state}$

2)

 

d) c) when not in the  $T_{\text{setup}}$

(like changing clk and d at the same time) our circuit becomes unstable and our outputs change forever.

but if we put a little bit of

delay in here (dt)


the circuit would work just fine as expected.

$\bar{Q}$  because our clk is positive edge.


b)

changing d while clk is active won't effect the output

 when d is 0/1, when clk becomes 1,  $\bar{Q}/Q$  after  $24 \text{ ns}$  becomes 1/0 and  $12 \text{ ns}$  after that,  $(12+24, 36 \text{ ns})$   $\bar{Q}/Q$  becomes 0/1.



3)

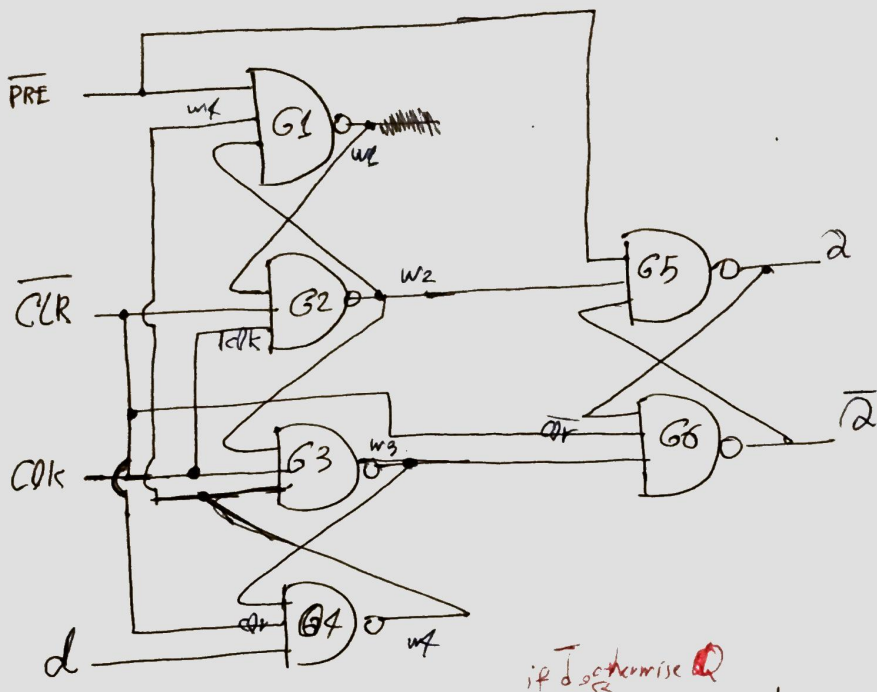

if  $\overline{Q}$  otherwise  $Q$

f) when  $clk$  is set to 1, after 24ns the  $\overline{Q}$  output changes and 12ns after that the  $Q$  input is changed. but when  $pre$  or  $clr$  inputs change, only 12ns after that  $Q/\overline{Q}$  output is changed (through  $G5$  NAND) on 12ns after that,  $\overline{Q}/Q$  output changes.

g) when  $pre$  or  $clr$  are active, our  $G5/G6$  conduct 0 to the  $Q/\overline{Q}$  outputs, no matter what our clock values are.

h) when both  $pre$  and  $clr$  are active,  $Q$  and  $\overline{Q}$  become 1 after 12ns (through  $G5$  or  $G6$ )

